

This laboratory assignment is due at the beginning of class on 2022/2/28.

Deliverables (revised): Please read the laboratory background and description for each portion and note all high-level tasks (underlined). A .zip/.tar file including the collection of all VHDL used to implement the lab and a document containing captures of simulation results and discussions for any questions posed in the lab must be submitted on Canvas. A detailed description of tasks performed and discussion of results is *not* required. The lab is a group assignment; all document submissions must also include a statement that clearly lists the responsibilities and contributions from group members. Lab groups must work together in the planning phase of the laboratory execution to determine each member's contributions. Lab groups will demonstrate compiled and loaded functionalities to the instructor during scheduled lab time. SignalTap functionality is optional.

Be advised: The laboratory assignment may be completed in groups sized 2-4. Only one graduate student is allowed per group. Groups are allowed to collaborate.

This laboratory exercise requires programming of the SoC FPGA using the DE10-Standard's on-board USB Blaster. To achieve this, the switches on SW10 must be configured according to Figure 1.

 


Figure 1: FPGA configuration mode MSEL setting for USB Blaster programming.

BACKGROUND

We wish to implement a finite state machine (FSM) that recognizes two specific sequences of applied input symbols, namely four consecutive 1s or four consecutive 0s. There is an input w and an output z . Whenever $w = 1$ or $w = 0$ for four consecutive clock pulses the value of z has to be 1; otherwise, $z = 0$. Overlapping sequences are allowed, so that if $w = 1$ for five consecutive clock pulses the output z will be equal to 1 after the fourth and fifth pulses. Figure 2 illustrates the required relationship between w and z .

 


Figure 2: Required timing for the output, z.

 


Figure 3: A state diagram for the FSM.

Name	State Code
	$y_8y_7y_6y_5y_4y_3y_2y_1y_0$
A	000000001
B	000000010
C	000000100
D	000001000
E	000010000
F	000100000
G	001000000
H	010000000
I	100000000

Table 1: One-hot codes for the FSM.

Name	State Code
	$y_8y_7y_6y_5y_4y_3y_2y_1y_0$
A	000000000
B	000000011
C	000000101
D	000001001
E	000010001
F	000100001
G	001000001
H	010000001
I	100000001

Table 2: Modified state codes for the FSM.

PART 1

A state diagram for this FSM is shown in Figure 3. For this part you will manually derive an FSM circuit that implements this state diagram, including the logic expressions that feed each of the state flip-flops. To implement the FSM use nine state flip-flops called y_8, \dots, y_0 and the one-hot state assignment given in Table 1.

DESIGN 1A

Design and implement the digital circuit using the one-hot state codes in Table 1 on the DE10-Standard board as follows:

- Create a new Quartus project for the FSM circuit by using the DE10-Standard's SystemBuilder tool. Select the appropriate hardware resources to create a template project that includes VHDL mappings for the LEDs, buttons, and switches.
 - The SystemBuilder tool can be acquired from Terasic's DE10-Standard download portal!
 - Go to <http://download.terasic.com/downloads/cd-rom/de10-standard/>, select DE10-Standard_v.1.0.1_SystemBuilder.zip

- The template project that is created will automatically generate a .qsf file for your project with all of the pin assignments needed to associate your VHDL code with the FPGA's physics pins!
- 2. Write a VHDL file that instantiates the nine flip-flops in the circuit and which specifies the logic expressions that drive the flip-flop input ports. Use only simple assignment statements in your VHDL code to specify the logic feeding the flip-flops. Note that the one-hot code enables you to derive these expressions by inspection. Use the toggle switch SW_0 as an active-low synchronous reset input for the FSM, use SW_1 as the w input, and the pushbutton KEY_0 as the clock input which is applied manually. Use the red light $LEDR_9$ as the output z , and assign the state flip-flop outputs to the red lights $LEDR_8$ to $LEDR_0$.
- 3. Include the VHDL file in your project and assign the pins on the FPGA to connect to the switches and the LEDs.
- 4. Simulate the behavior of your circuit by designing a test bench that exercises all FSM states and valid operating conditions.
- 5. Once you are confident that the circuit works properly as a result of your simulation, complete design compilation. Load your design to the FPGA using the Programmer button. Your design must include both the 5CSXFC6D6F31C6N device with associated .sof file *and* a component called SOCVHPS to properly load your design. This can be achieved by selecting Auto Detect in the programmer, followed by the appropriate FPGA device (you may need to add the .sof file to your FPGA device entry using the Change File button).
- 6. Test the functionality of your design by applying the input sequences and observing the output LEDs. Make sure that the FSM properly transitions between states as displayed on the red LEDs, and that it produces the correct output values on $LEDR_9$.
 - Optional: To include SignalTap functionality, complete compilation only through to the appropriate step (Analysis and Synthesis). Once this functionality is added to your design, complete the full compilation and load the design onto the FPGA chip

DESIGN 1B

It is often desirable to set all flip-flop outputs to the value 0 in the reset state. Table 2 shows a modified state assignment in which the reset state, A, uses all 0s. The design is achieved by inverting the state variable y_0 .

Design and implement the digital circuit using the modified state codes in Table 2 on the DE10-Standard board as follows:

1. Create a new Quartus project for the FSM circuit similar to Design 1A.
2. Repeat steps 2-6 that were performed for Design 1A.
Hint: you should need to make very few changes to the logic expressions in your circuit to implement the modified state assignment.)

PART 2

For this part you are to write another style of HDL code for the FSM in Figure 3. In this version of the code you should not manually derive the logic expressions needed for each state flip-flop. Instead, describe the state table for the FSM by using a VHDL CASE statement in a PROCESS block, and use another PROCESS block to instantiate the state flip-flops. You can use a third PROCESS block or simple assignment statements to specify the output z . To implement the FSM, use four state flip-flops y_3, \dots, y_0 and binary codes, as shown in Table 3.

Name	State Code $y_3y_2y_1y_0$
A	0000
B	0001
C	0010
D	0011
E	0100
F	0101
G	0110
H	0111
I	1000

Table 3: Binary state codes for the FSM.

```

library ieee;
use ieee.std_logic_1164.all;
entity part2 is
port(. . . -- define input and output ports
);
end part2;
architecture rtl of part2 is
. . . -- declare signals
type State_type is (A, B, C, D, E, F, G, H, I);
-- Attribute to declare a specific encoding for the states
attribute syn_encoding : string;
attribute syn_encoding of State_type : type is "0000 0001 0010 0011 0100
0101 0110 0111 1000";
signal y_Q, Y_D : State_type; -- y_Q is present state, y_D is
-- next state
begin
. . .
process (w, y_Q) -- state table
begin
case y_Q is
when A =>
if (w = '0') then Y_D <= B;
else Y_D <= F; end if;
. . . -- other states
end case;
end process;
process (clock) -- state flip-flops
begin
. . .
end process;
. . . -- assignments for output z and the leds
end rtl;

```

Figure 4: Skeleton VHDL code for the FSM.

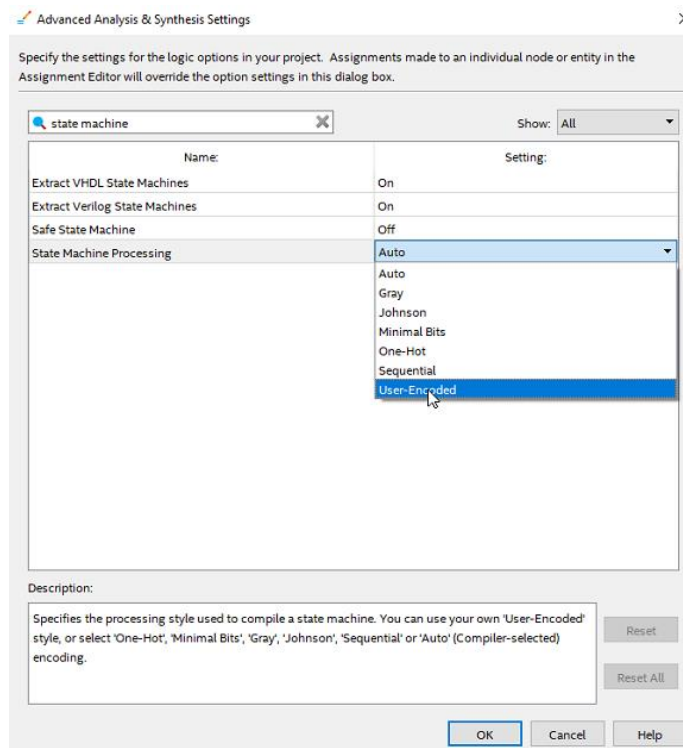


Figure 5: Specifying the state assignment method in Quartus.

Implement your design as follows:

1. Create a new project for the FSM similar to designs in Part 1.
2. Include in the project your VHDL file that uses the style of code in Figure 4. Use the same switches, pushbuttons, and lights that were used in Part 1.
3. Before compiling your code it is necessary to explicitly tell the Synthesis tool in Quartus that you wish to have the finite state machine implemented using the state assignment specified in your VHDL code. If you do not explicitly give this setting to Quartus, the Synthesis tool will automatically use a state assignment of its own choosing, and it will ignore the state codes specified in your VHDL code. To achieve this setting, choose Assignments > Settings in Quartus, and click on the Compiler Settings item on the left side of the window, then click on the Advanced Settings (Synthesis) button. As indicated in Figure 5, change the parameter State Machine Processing to the setting User-Encoded.
4. Compile your project and **optionally** add SignalTap functionality. To examine the circuit produced by Quartus open the RTL Viewer tool. Double-click on the box shown in the circuit that represents the finite state machine and determine whether the state diagram that it shows properly corresponds to the one in Figure 3. To see the state codes used for your FSM, open the Compilation Report, select the Analysis and Synthesis section of the report, and click on State Machines.
5. Download the design into the FPGA chip and test its functionality.
6. In step 3 you instructed the Quartus Synthesis tool to use the state assignment given in your VHDL code. To see the result of removing this setting, open again the Quartus settings window by choosing Assignments > Settings, and Compiler Settings item on the left side of the window, then click on the Advanced Settings (Synthesis) button. Change the setting for State Machine Processing from User-Encoded to One-Hot. Recompile the circuit and then open the report file, select the Analysis and Synthesis section of the report, and click on State Machines. Compare the state codes shown to those given in Table 2 and discuss any differences that you observe.

PART 3

The sequence detector can be implemented in a straightforward manner using shift registers, instead of using the more formal approach described above. Create VHDL code that instantiates two 4-bit shift registers; one is for recognizing a sequence of four 0s, and the other for four 1s. Include the appropriate logic expressions in your design to produce the output z. Make a Quartus project for your design and implement the circuit on your DE10-Standard board. Use the switches and LEDs on the board in a similar way as you did for Parts 1 and 2 and observe the behavior of your shift registers and the output z.

Answer the following question: could you use just one 4-bit shift register, rather than two? Explain your answer.

PART 4 – OPTIONAL & EXTRA CREDIT

In this part of the exercise you are to implement a Morse-code encoder using an FSM. Morse code uses patterns of short and long pulses to represent a message. Each letter is represented as a sequence of dots (a short pulse), and dashes (a long pulse). The first eight letters of the alphabet are represented using such dot-dash combinations as depicted in Figure 6.

A	• —
B	— • • •
C	— • — •
D	— • •
E	•
F	• • — •
G	— — •
H	• • • •

Figure 6: Dot-dash glossary for the first eight letters in the English alphabet.

Design and implement a Morse-code encoder circuit using an FSM, including simulations and SignalTap as described in Parts 1-3. Your circuit should take as input one of the first eight letters of the alphabet and display the Morse code for it on a red LED. Use switches SW_{2-0} and pushbuttons KEY_{1-0} as inputs. When a user presses KEY_1 , the circuit should display the Morse code for a letter specified by SW_{2-0} (000 for A, 001 for B, etc.), using 0.5-second pulses to represent dots, and 1.5-second pulses to represent dashes. Pushbutton KEY_0 should function as an asynchronous reset.

A high-level schematic diagram of a possible circuit for the Morse-code encoder is shown in Figure 7.

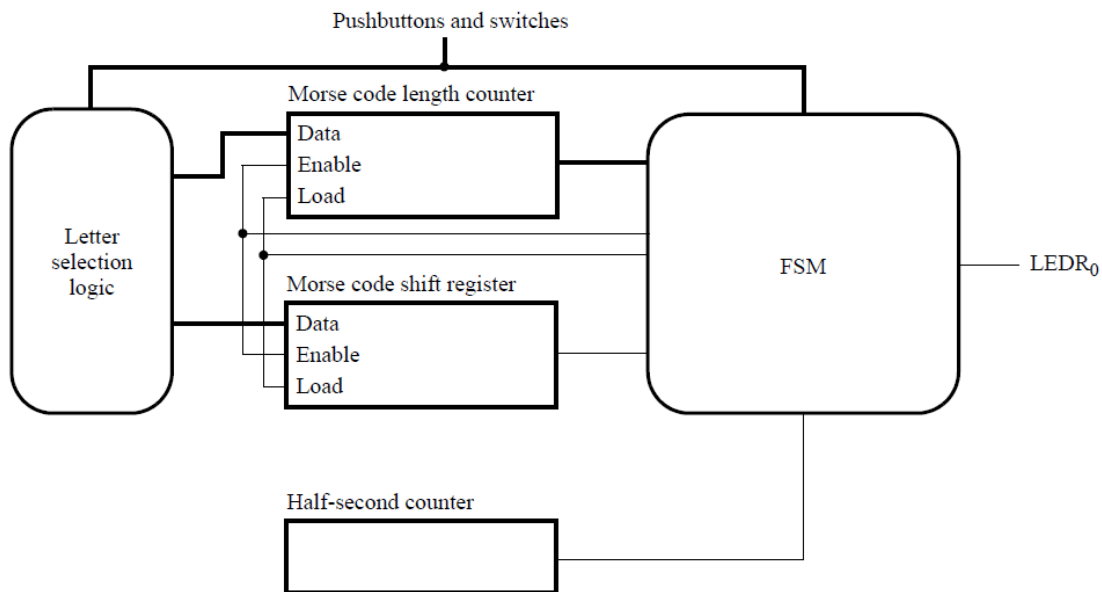


Figure 7: High-level schematic diagram of the circuit for Part 4.